

# Memory Circuits & Systems

## Exercise 1

### Static Noise Margin of SRAM


**Professor Po-Tsang Huang**

**International College of Semiconductor Technology  
National Yang Ming Chiao Tung University**


 
# FinFET SRAM



- In FinFET, the width which is given by  $W = (T_{\text{FIN}} + 2H_{\text{FIN}}) \times N_{\text{FIN}}$  is quantized.
- For a high-density FinFET 6T-SRAM cell and a high-performance FinFET 6T-SRAM cell, the width ratio of Pull-Up PMOS, pass-gate NMOS and Pull-down NMOS are 1:1:1 and 1:2:2, respectively



Fin-based SRAM bitcell design

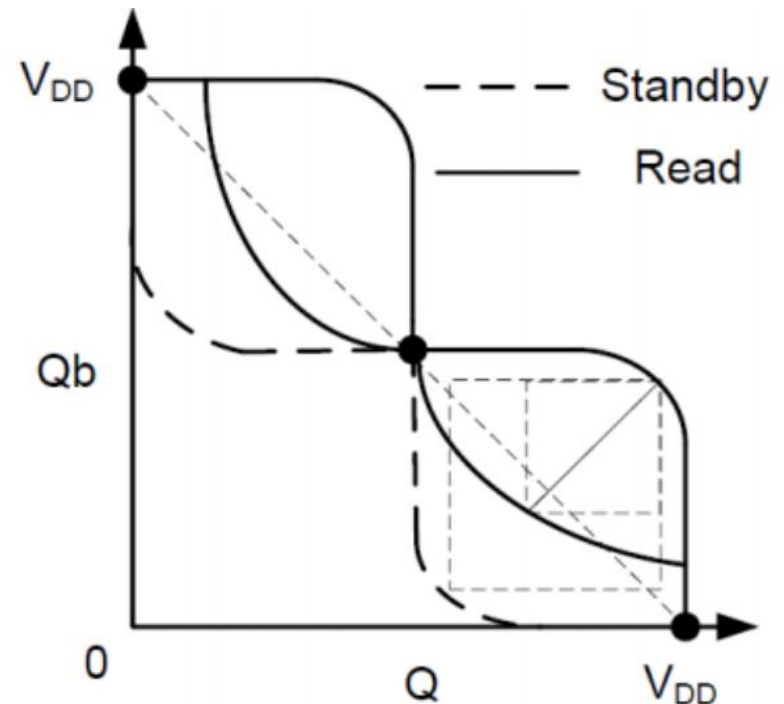
 
## Butterfly Curve of SNM and RSNM [30%]

- Using 7nm FinFET model to analyze SNM and RSNM of 1:1:1 and 1:2:2 FinFET SRAM cells
- ◆ Plot butterfly curve of data retention and read modes
  - Hint: DC analysis and get data by .print


 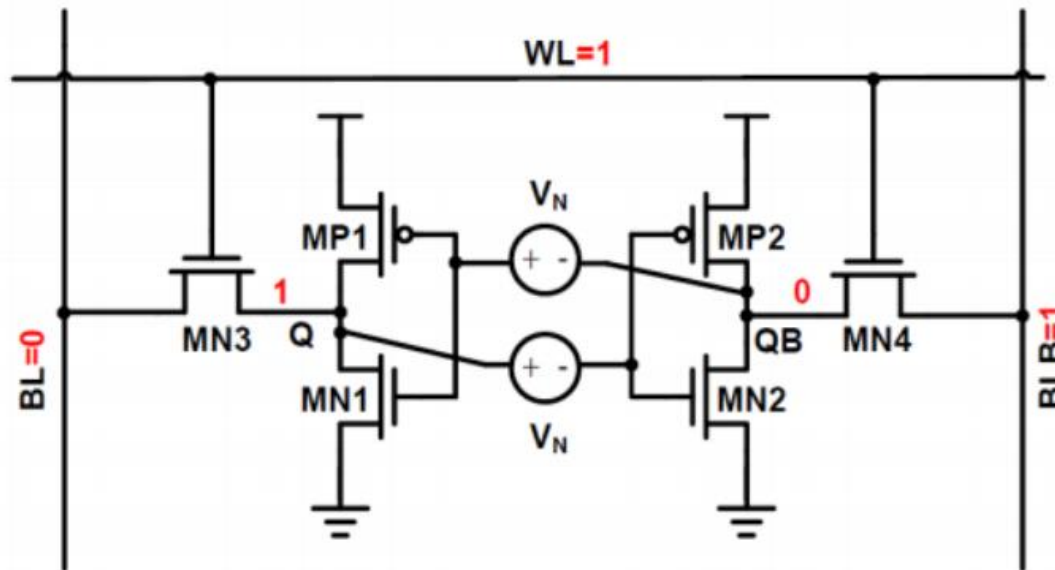
# Write Noise Margin (WNM) Curve [30%]

- Using 7nm FinFET model to analyze WNM of 1:1:1 and 1:2:2 FinFET SRAM cells
- ◆ Measure the transfer curve of the inverter and plot the curve



# Static Noise Margin Analysis [40%]

---

- Analyze SNM, RSNM and WNM of 1:1:1 and 1:2:2 FinFET SRAM cells under
  - ◆ different supply voltages from 0.7V to 0.4V
    - Bitline/wordline voltages are the same as that of cell voltage
  - ◆ different wordline voltages
    - 0.9V to 0.5V when  $V_{DD} = 0.7V$

# Submission on e3 platform

---

- Please compress your **report & source codes in a single compressed file (.zip/.rar)** and upload this single file on E3 platform
- Naming rules of the compressed file
  - ◆ Upload file: **Ex1\_#ID.zip (including report & source code)**
- Due date: 3/28 PM 23:55