

Memory Circuits & Systems

Exercise 3

Sensing Amplifier

Professor Po-Tsang Huang


**International College of Semiconductor Technology
National Yang Ming Chiao Tung University**



Design & Analysis of Sensing Amplifier


- Implementation read operation of SRAM using 7nm FinFET model (frequency = 1GHz)
 - ◆ Input: PRE, WL, SEN, C-SEL
 - ◆ Output: dout
 - ◆ Design three types of sensing amplifiers and simulate 1 column with 512 SRAM cells
 - Current-mode SA
 - Voltage-mode SA
 - Voltage mode SA with pre-charging circuits
 - ◆ Estimate loading of BL and BLB (cells + wire loading)
 - ◆ Please compare and analyze the performance in terms of read power and sensing timing of the 3 sensing amplifiers

Data Sensing for Read Operation of SRAM

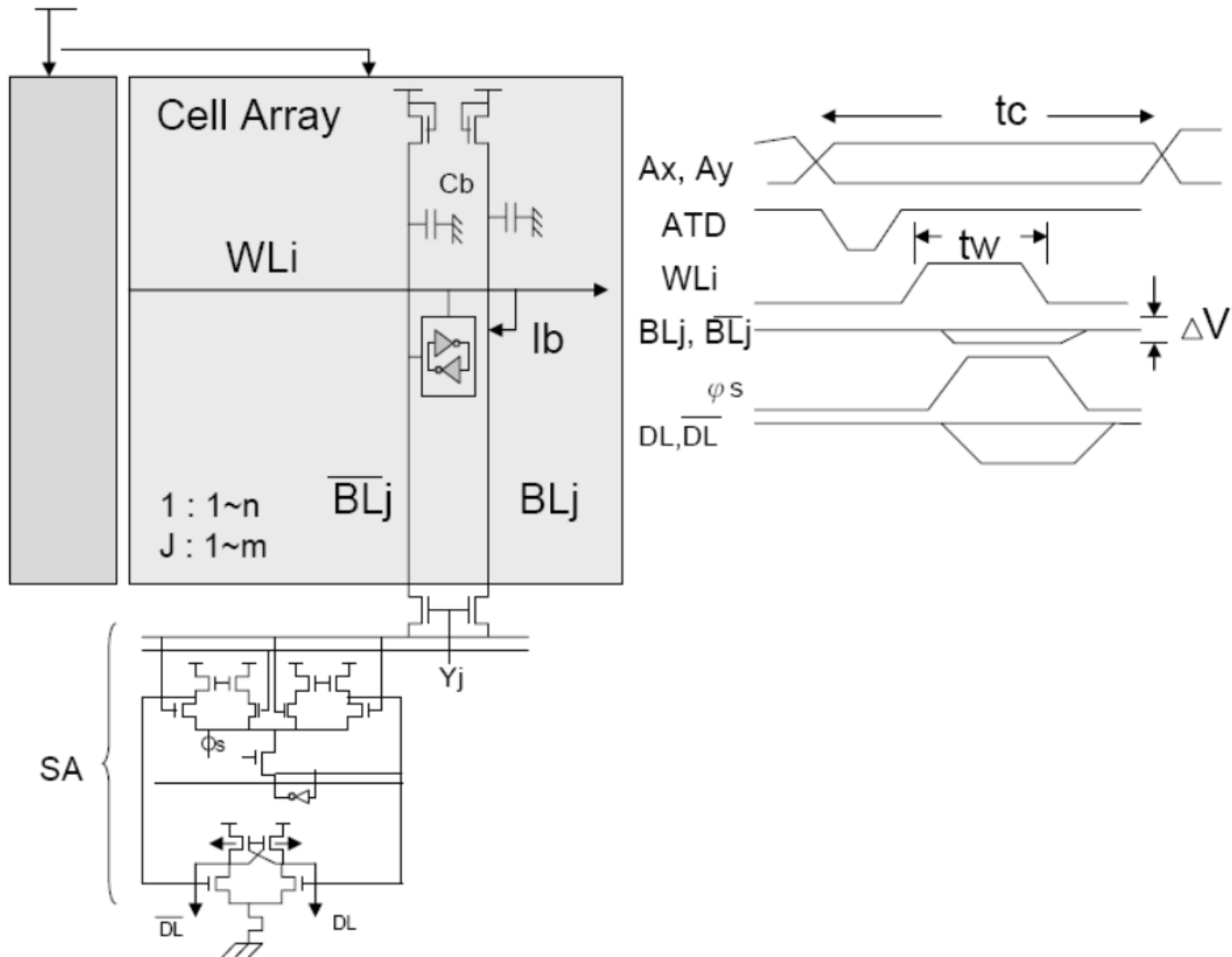

Read mode of SRAM

 - Step 1:
 - ◆ BL and BLB precharged by precharger
- Step2:
 - ◆ Activate WL of the selected row
- Step3:
 - ◆ Depend on the data of the selected cell, BL or BLB discharged by the pull down NMOS
- Step4:
 - ◆ Enable the sense amplifier
- Step5:
 - ◆ Sense read data



Submission on E3 platform

- Please compress your **report & source codes in a single compressed file (.zip/.rar)** and upload this single file on E3 platform
- ◆ **Report: simulation results(read power & sensing timing), comparison and analysis of 3 Sensing Amplifiers**
- ◆ Naming rules of the compressed file
- ◆ Upload file: **Ex3_#ID.zip (including report & source code)**
- Due date: 4/25 P.M. 23:55